

## VR-RDC30xx DC/DC Converter Voltage Regulator module

In many cases where a single, high voltage is available like in high power Class-D designs, there are also low voltages required. Normally, people use a small separate power supply for that.

With this series of Voltage Regulator modules we use a professional DC/DC converter range, capable of transferring relative high voltages into regulated lower voltage(s) for low power electronics like preamplifiers, DAC's and digital circuits. So with these modules you only need a single supply now.

The range of 30W DC/DC converters as we use have a very wide input voltage range and are available as single 3,3V, 5V, 12V and 15V, symmetrical with  $\pm 5V$ ,  $\pm 12V$  or  $\pm 15V$  and even triples with 3,3V or 5V as well. The professional converter module is metal encapsulated and very small considering what its capable of. These switch mode modules are, unlike many others, doing all required in one on a high quality scale.

While developing our PS-UNxx Power Supply modules we wanted that these would have an option making it possible to get an extra, low voltage regulated output(s) as well. This can only be done by the use of switching DC/DC converter modules. They are available with one up to three regulated secondary voltages.


About regardless the input voltage and supply type, you now can have high quality symmetrical supply voltages for analogue electronics and/or voltages for digital circuits as well without extra electronics other than this VR-RDC-30 module connected to a supply. We made them pin-compatible with our linear regulators. All our NEW switched mode Voltage Regulator modules fit on about all our ELTIM Power Supplies while using the versions with a 2x 26 pole header. While using the screw terminal version you can use them anywhere.

- Highlights of this VR-JTL30 Converter/Voltage Regulator module:
  - Tiny 1" x 2" [RDC30 DC/DC converter / regulator module](#) with 30W capacity.
  - Professional quality with expected MTBF of 320000 hours.
  - Extremely high efficiency of up to 91%, switching at 270kHz with very low RF-residue.
  - Very wide input voltage ranges of 36 – 140Vdc and 55 – 176Vdc.
  - Supplying input voltage can be single line or symmetrical (  $-V + +V = V_{in}$  ).
  - Input and output circuits galvanic separated, can be overruled by a jumper wire / main PCB track.
  - Output single voltage variants: 3,3V; 5V; 12V; 15V.
  - Outputs symmetrical output variants:  $\pm 5V$ ;  $\pm 12V$ ;  $\pm 15V$ .
  - Outputs triple output variants:  $+3,3/\pm 12V$ ;  $+3,3/\pm 15V$ ;  $+5/\pm 12V$ ;  $+5/\pm 15V$ .
  - Secondary overvoltage, over temperature (@115°C) and overload protection @150%.
  - All outputs are regulated independently within 0,2% accuracy and high dynamics.
  - Versions with a straight or angled header connector (3A pins). Fit on all our [PS-Unxx\(S\) Supplies](#).


For every output connection 6 pins are used, so  $6 \times 3A = 18A$  (over)rated.

Pinning is compatible with our linear regulated VR-modules.

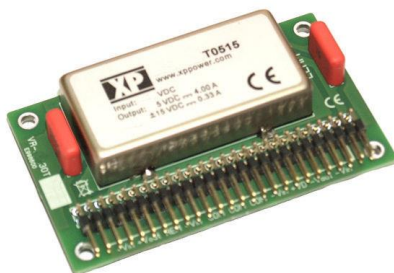- Versions with a 10A screw terminal and 4x M3 holes for separate module mounting.
- PCB tracks and header/screw terminal calculated to handle 10A+ per output voltage.
- Professional FR4 board with dimensions of 75x45x12mm.



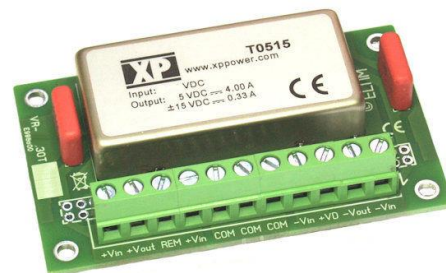Models with 2x 26 pins matching other [ELTIM VR-modules](#)



Models with 11-pole screw terminal and 4x M3 holes

With the triple versions there is an extra output available as +VD (for digital. 3,3V or 5V).

## Converter / regulator module

We decided to use the professional DC/DC converter / regulator modules from XP-Power, due to a long lifespan, high switching frequency and very high efficiency. Besides that, these modules are capable of handling high input voltages as we need in order to be able to connect them to the quite high voltages of audio power amplifiers as we had in mind. The ones we use are of a different league and are allowed to use in f.e. industrial equipment, locomotives, etc.

The life span (MTBF, Mean Time Between Failures) is **320000 hours** (45 years, 24/7) for single/dual versions. The triplets last 320000 hours "only". So, about a human lifetime. The efficiency is over **90%**. The irregularly high switching frequency of **270kHz** leaves hardly any residue, and what's left will do no harm.

If you want it all, this high frequency residue and its harmonics can be filtered out most easy with an LC-filter.



The switching modules we use are capable of transferring quite high DC-voltages (as f.e. used in class-D power amplifiers already) into a range of low voltages (see table below) used in preamplifiers, DAC's, DSP's, etc. So with these, you can combine the instant and solid power from a linear (single or symmetrical) power supply AND have clean voltage(s) for the driving electronics in one supply. Just as we believe is a missing link so far. Finally class-D makes sense regarding linear efficiency and punch power. Read our [comments](#) about that.

## Availability and pinning of output voltages

There are two input voltage ranges available **36-140Vdc** (+Vin <> -Vin), 72V nom. and **55-176Vdc**, 110V nom.

Header	26 ab	25 ab	24 ab	23 ab	22 ab	21-22 ab	19 ab	18–9 ab				8 ab	7 ab	6 ab	5 ab	4 ab	3 ab	2 ab	1 ab	
Screw con.	11	10 (V1)				-	9	8	7	6	5	4	3 (V3)			2 (V2)			1	
Input voltage range 36 – 140Vdc, 72V nominal																				
RDC3072S3V3	+Vin	3,3V (7,5A)				n.c.	Remote	+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC3072S05	+Vin	5V (6,0A)				n.c.		+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC3072S12	+Vin	12V (2,5A)				n.c.		+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC3072S15	+Vin	15V (2,0A)				n.c.		+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC3072D05	+Vin	+5V (3,0A)				n.c.		+Vin	COM		-Vin		n.c			-5V (3,0A)			-Vin	
RDC3072D12	+Vin	+12V (1,25A)				n.c.		+Vin	COM		-Vin		n.c			-12V (1,25A)			-Vin	
RDC3072D15	+Vin	+15V (1,0A)				n.c.		+Vin	COM		-Vin		n.c			-15V (1,0A)			-Vin	
RDC3072T0312	+Vin	+12V (0,42A)				n.c.		+Vin	COM		-Vin		+3,3V (5,0A)			-12V (0,42A)			-Vin	
RDC3072T0315	+Vin	+15V (0,33A)				n.c.		+Vin	COM		-Vin		+3,3V (5,0A)			-15V (0,33A)			-Vin	
RDC3072T0512	+Vin	+12V (0,42A)				n.c.		+Vin	COM		-Vin		+5V (4,0A)			-12V (0,42A)			-Vin	
RDC3072T0515	+Vin	+15V (0,33A)				n.c.	+Vin	COM		-Vin		+5V (4,0A)			-15V (0,33A)			-Vin		
Input voltage range 55 – 176Vdc, 110V nominal																				
RDC30110S3V3	+Vin	3,3V (7,5A)				n.c.	Remote	+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC30110S05	+Vin	5V (6,0A)				n.c.		+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC30110S12	+Vin	12V (2,5A)				n.c.		+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC30110S15	+Vin	15V (2,0A)				n.c.		+Vin	COM		-Vin		n.c			Trim			-Vin	
RDC30110D05	+Vin	+5V (3,0A)				n.c.		+Vin	COM		-Vin		n.c			-5V (3,0A)			-Vin	
RDC30110D12	+Vin	+12V (1,25A)				n.c.		+Vin	COM		-Vin		n.c			-12V (1,25A)			-Vin	
RDC30110D15	+Vin	+15V (1,0A)				n.c.		+Vin	COM		-Vin		n.c			-15V (1,0A)			-Vin	
RDC30110T0312	+Vin	+12V (0,42A)				n.c.		+Vin	COM		-Vin		+3,3V (5,0A)			-12V (0,42A)			-Vin	
RDC30110T0315	+Vin	+15V (0,33A)				n.c.		+Vin	COM		-Vin		+3,3V (5,0A)			-15V (0,33A)			-Vin	
RDC30110T0512	+Vin	+12V (0,42A)				n.c.		+Vin	COM		-Vin		+5V (4,0A)			-12V (0,42A)			-Vin	
RDC30110T0515	+Vin	+15V (0,33A)				n.c.	+Vin	COM		-Vin		+5V (4,0A)			-15V (0,33A)			-Vin		

## Remote controlled function

Pin 9 (REMOTE) can be left open for normal operation. The unit comes in after 30mS typical. For remote control, delayed power on, resp. fast power off connect 9(REM) to 1(-Vin).

## Trimming

The single voltage variant can be trimmed 10% by use of a resistor between pin 6 and 7 OR 6 and 8. Please check the [RDC30 datasheet](#) for details.

### Galvanic separation

Without further precautions/actions, the input and output(s) are galvanic separated, see fig. 1 at next page. In this case both electronic devices run independently and the “guest” is just extracting energy from the “host”. This could be useful in f.e. your car or boat. Just extracting energy from the battery. However, this RDC30 runs on higher input voltages than most batteries are. In that case, use [VR-JLT30 modules](#) (9-36Vdc in). These have the same size and output data as this RDC30 module range.

In order to drop the galvanic separation, meaning connecting the grounds of both devices, a link has to be made between the both grounds. We made internal connections on our modules for simple linking:

- For symmetrical host supplies: Just connect **GND** of the host to **COM** of our module (Fig 2) as seems logical. While using our symmetrical Power Supply modules, we already made this link on the PS-board. Just mount this VR-RDC30 module on the header location on the PS-module and all works.
- For single, positive voltage host supplies: link **-Vin** (=Host GND) with **COM** of our module (fig 3). While using our single voltage Power Supply modules, we already made this link on the PS-board. Just mount this VR-RDC30 module on the header location on the PS-module and all works.
- For single, negative voltage host supplies: link **+Vin** (=Host GND) with **COM** of our module (fig 4). This situation hardly occurs, but sometimes in very old installations or very special equipment.

While using a header version of our module, link 1ab (for pos. supplies) or 26ab (neg. supplies) to 8-18ab on the mother PCB as we have done on our power supply modules already.

While using a symmetrical host supply, just connect header COM pins 9-18ab to GND of the host PCB.

At the last page we show some examples of this jumper wiring.

Actually we sell this module most, since it is capable of the following:

- High input voltage, up to 176Vdc (or  $\pm 88$ Vdc) together with
- High output current single voltage for digital circuits
- Acceptable symmetrical outputs for High-End analogue audio circuits
- Triple output voltages with sufficient current capabilities for combined analogue and digital circuitry
- Still a very compact size

***These designs are copyrighted by  
ELTIM audio BV, Louis Timmers 2019 ©  
PE1LTM***

## Examples of connecting ELTIM switched mode regulator modules:

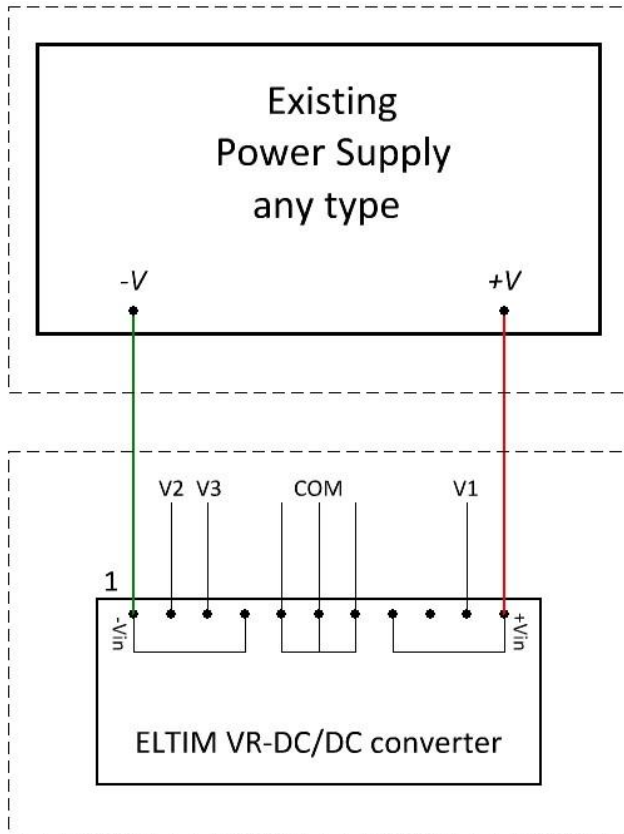


Fig 1: Galvanic separated host / guest supplies

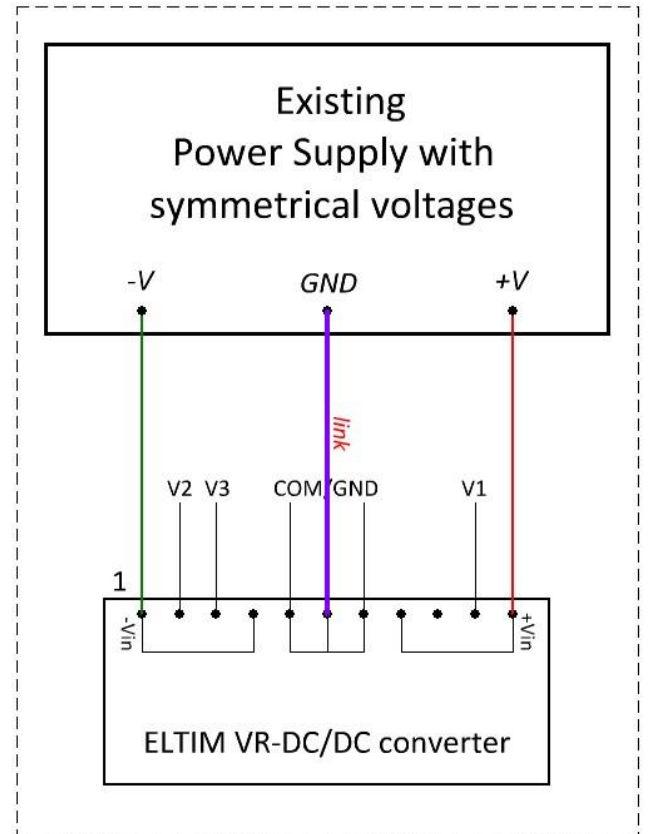


Fig 2: Symmetrical host supply, with common ground

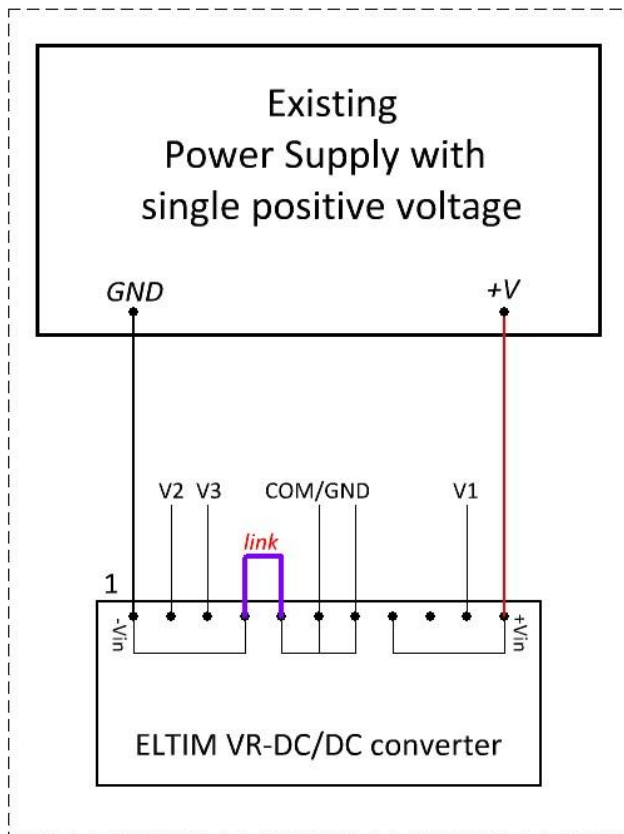


Fig 3: Single positive supply host, with common ground

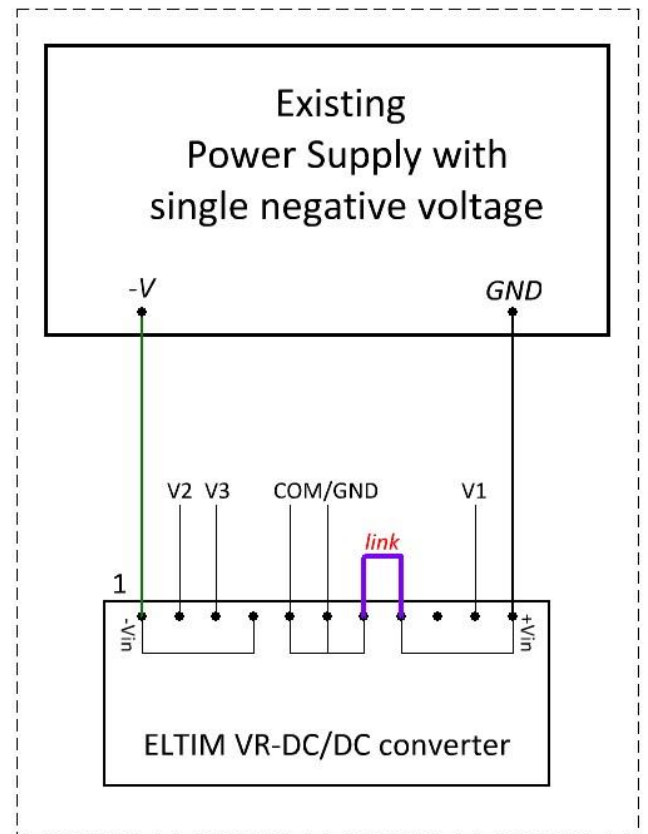


Fig 4: Single negative supply host, with common ground